

```
1 # Instrumentation Design 1
2 ## Lab 4 - Loaded Voltage and Current Divider Circuits
3
4 Lab report by Matt Rixman
```

```
1 ### 1. Loaded Voltage Divider Circuits
2
3 Objective 1: To find what effect load has on the voltage relationships in a
  voltage-divider circuit
4
5 Objective 2: To verify the results of objective 1 by experiment
```

```
In [1]: 1 class Ohms:
        2     r1 = r2 = r3 = 1.2e3 #  $\Omega$ 
```

1. The above resistors were connected to match figure 1.3(a)


2. At 10V the following values were measured

From Point	To Point	Measured Voltage (V)
B	D	6.7
C	D	3.4

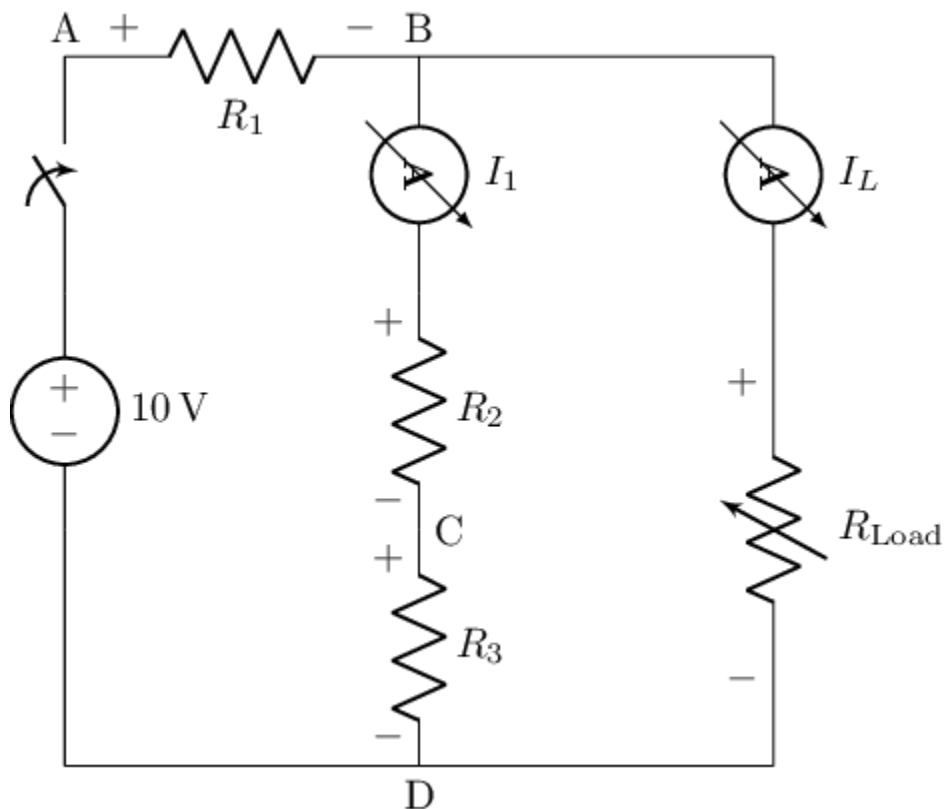3-8. A potentiometer was added connecting points B and D and varied to match certain currents through the load. Here is a redrawing of figure 1.3 (b) that makes the meshes more obvious:

In [2]:

```
1 from lcapy import Circuit
2 cct = Circuit("""
3 V 0 12 {10}; down
4 SW 0 1 no; up
5 W 2 3; right=1.5
6 R1 1 2 {1200}; right=1.5, v=_, l=R_1
7 AM1 3 4; down, l=I_L
8 R_L 4 8; down=2, variable, l=R_{Load}, v=
9 AM2 10 6; down, l=I_1
10 R2 6 7 {1200}; down, v=_, l=R_2
11 R3 7 11 {1200}; down, v=_, l=R_3
12 W 11 8; right
13 W 11 9; left
14 W 9 12; up
15 A1 1; l=A, anchor=south
16 A2 2; l=B, anchor=south
17 A3 7; l=C, anchor=west
18 A4 11; l=D, anchor=north
19 """)
20 cct.draw(label_ids=False, draw_nodes=False, label_nodes=False)
```



The potentiometer was adjusted to achieve the load currents (I_L) below, and values were measured. They're listed in step 9 for easy comparison

9. Calculations

First we write expressions for our resistors as voltage deltas in terms of clockwise mesh currents (I_{left} , and I_{right})

In [3]:

```
1 # nothing to see here
2 from si_prefix import si_format as f # used in table renderings
3 from sympy import symbols, Eq       # used for algebra
4 from sympy.solvers import solve
5 from IPython.display import display
6 r1, r2, r3, rload, rtot = symbols('R_1, R_2, R_3, R_load, R_total')
7 vpwr, vab, vbc, vbd, vcd = symbols('V_pwr, V_ab, V_bc, V_bd, V_cd')
8 ileft, iright, ibleeder = symbols('I_left, I_right, I_bleeder')
9
10 # Ohm's law gives equations for each individual voltage drop
11 vab_r1 = r1 * (-ileft)
12 display(Eq(vab, vab_r1))
13
14 vbc_r2 = r2 * (-ileft + iright)
15 display(Eq(vbc, vbc_r2))
16
17 vcd_r3 = r3 * (-ileft + iright)
18 display(Eq(vcd, vcd_r3))
19
20 vbd_rload = rload * (-iright)
21 display(Eq(vbd, vbd_rload))
22
```

$$V_{ab} = -I_{\text{left}} R_1$$

$$V_{bc} = R_2 (-I_{\text{left}} + I_{\text{right}})$$

$$V_{cd} = R_3 (-I_{\text{left}} + I_{\text{right}})$$

$$V_{bd} = -I_{\text{right}} R_{\text{load}}$$

Then we write equations for those mesh currents in terms of the voltage deltas.

In [4]:

```
1 # clockwise from power supply
2 left_mesh = Eq(ileft, solve(Eq(0, sum([vpwr, vab_r1, vbc_r2, vcd_r3])), ileft))
3 display(left_mesh)
4
5 # clockwise from B
6 right_mesh = Eq(iright, solve(Eq(0, sum([vbd_rload, -vbc_r2, -vcd_r3])), iright))
7 display(right_mesh)
```

$$I_{\text{left}} = \frac{I_{\text{right}} R_2 + I_{\text{right}} R_3 + V_{\text{pwr}}}{R_1 + R_2 + R_3}$$

$$I_{\text{right}} = \frac{I_{\text{left}} (R_2 + R_3)}{R_2 + R_3 + R_{\text{load}}}$$

Solve the above equations as a system, include other equations to get derived values

```

In [5]: 1 def evaluate_at(iloading_amps):
2         return solve([
3             # solve for currents
4             left_mesh, right_mesh,
5
6             # bleeder is superposition of left and right mesh currents
7             # (which are in opposite directions)
8             Eq(ibleeder, ileft - iright),
9
10            # derive voltages
11            Eq(vcd, vcd_r3),
12            Eq(vbd, vbd_rload),
13
14            # substitute values for symbols
15            Eq(iright, iload_amps),
16            Eq(r1, Ohms.r1),
17            Eq(r2, Ohms.r2),
18            Eq(r3, Ohms.r3),
19            Eq(vpwr, 10), # volts
20        ])[0]
21
22 at_load = { 2: evaluate_at(2e-3),
23            4: evaluate_at(4e-3),
24            6: evaluate_at(6e-3) } # referenced in the table below

```

Measured Values

Load Current (A)	Bleeder Current I_1 (A)	B-D Voltage (V)	C-D Voltage (V)	Load Resistance (Ω)
2m	2.07m	-5.08	-2.96	2.45k
4m	1.35m	-3.98	-1.67	780
6m	0.77m	-1.90	-0.95	314

Calculated Values

Load Current (A)	Bleeder Current I_1 (A)	B-D Voltage (V)	C-D Voltage (V)	Load Resistance (Ω)
2m	2.1 m	-5.1	-2.5	2.5 k
4m	1.4 m	-3.5	-1.7	866.7
6m	777.8 μ	-1.9	-933.3 m	311.1

10. a) As the load resistance decreases, the bleeder voltage also decreases.

b,c) Decreasing the load resistance $2500\Omega \rightarrow 866\Omega \rightarrow 311\Omega$ caused the load current to increase $2\text{mA} \rightarrow 4\text{mA} \rightarrow 6\text{mA}$ and the bleeder current to decrease $2.1\text{mA} \rightarrow 1.4\text{mA} \rightarrow 0.78\text{mA}$. When we do this, we increase both the overall current that the circuit draw, and the proportion of that current that makes it through the load relative to the bleeder.

d) Increasing the load current $2\text{mA} \rightarrow 4\text{mA} \rightarrow 6\text{mA}$ reduced the total divider tap voltage $5.1\text{V} \rightarrow 3.5\text{V} \rightarrow 1.9\text{V}$. This is because the available current is given an increased opportunity to "flow around" the divider, rather than through it, thus causing a reduced potential across it.

e) Our results compare favorably with the experimental data, (although it looks like we may have bumped the potentiometer sometime while taking measurements for the 4mA sample).

2. Designing Voltage-and-Current Divider Circuits

Objective 1: To design a voltage divider that will meet specified voltage and current requirements

Objective 2: To design a current divider that will meet specified current and voltage requirements

Objective 3: To construct and test circuits to see that they meet the design requirements

A: Voltage Divider Circuit

We designed a circuit which accepts a 15V power supply and delivers 9V to two parallel branches. It aims to deliver 3mA to the "load" branch, and 0.3mA to the "bleeder" branch. It uses the following resistors.

In [6]:

```
1 r1 = 1.5e3
2 rbleeder = 30e3
3 rload = 3e3
4
5 r_bc = 1 / (1/rbleeder + 1/rload)
6 r_total = r1 + r_bc
7 i_total = 15 / r_total
8 v_ab = 15 * r1 / r_total
9 v_bc = 15 * r_bc / r_total
10 print("V_ab =", f(v_ab, precision=2))
11 print("V_bc =", f(v_bc, precision=2))
12 print("I_tot =", f(i_total, precision=2))
```


V_ab = 5.32

V_bc = 9.68

I_tot = 3.55 m

In [7]:

```
1 cct = Circuit("""
2 V 1 11 {15}; down
3 W 1 1_1; up=0.5
4 W 3 3_1; up=0.5
5 P 1_1 3_1; right, v=5.3 V
6 R1 1 3; right=1.5
7 W 3 4; down
8 W 3 6; right=1.5
9 W 6 5; down
10 Rbleeder 4 8 ; down
11 Rload 5 9 ; down
12 W 6 6_1; right=1.5
13 W 12 12_1; right=1.5
14 P 6_1 12_1; down, v=9.68 V
15 W 10 12; right
16 W 12 9; up
17 W 8 10; down
18 SW 11 10 no; right
19 A1 1; l=A, anchor=south east
20 A2 3; l=B, anchor=south east
21 A4 10; l=C, anchor=south east
22 """)
23 cct.draw(label_ids=False, draw_nodes=False, label_nodes=False)
```

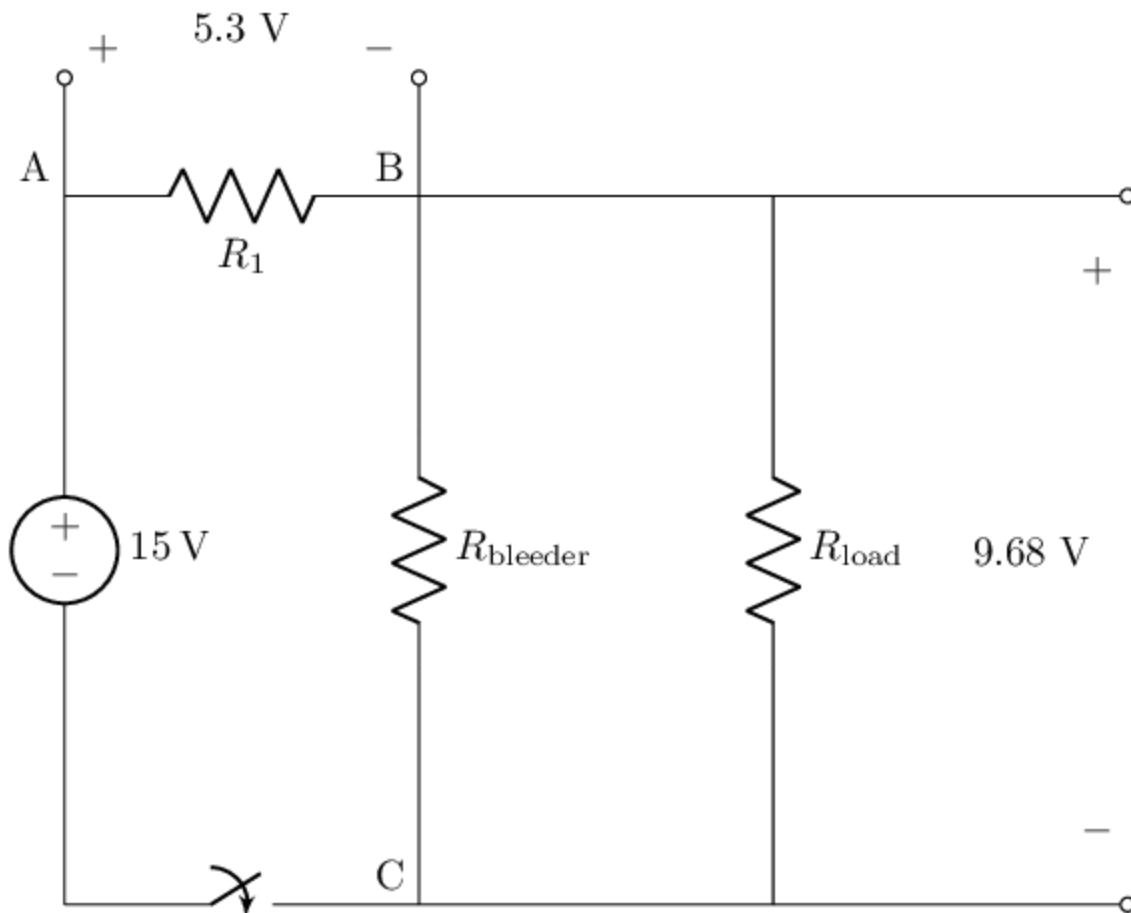

```
In [8]: 1 r1, rbleeder, rload = symbols('R_1, R_bleeder, R_load')
2 vpwr, vab, vbc = symbols('V_pwr, V_ab, V_bc')
3 ileft,  iright, ibleeder = symbols('I_left, I_right, I_bleeder')
4
5 # Ohm's law gives equations for each individual voltage drop
6 # in terms of mesh currents
7 vab_r1 = r1 * (-ileft)
8 display(Eq(vab, vab_r1))
9
10 vbc_rbleeder = rbleeder * (-ileft + iright)
11 display(Eq(vbc, vbc_rbleeder))
12
13 vbc_rload = rload * (-iright)
14 display(Eq(vbc, vbc_rload))
15
16 # clockwise from power supply
17 left_mesh = Eq(ileft, solve(Eq(0, sum([vpwr, vab_r1, vbc_rbleeder])), ileft))
18 display(left_mesh)
19
20 # clockwise from B
21 right_mesh = Eq(iright, solve(Eq(0, sum([vbc_rload, -vbc_rbleeder])), iright))
22 display(right_mesh)
```

$$V_{ab} = -I_{\text{left}} R_1$$

$$V_{bc} = R_{\text{bleeder}} (-I_{\text{left}} + I_{\text{right}})$$

$$V_{bc} = -I_{\text{right}} R_{\text{load}}$$

$$I_{\text{left}} = \frac{I_{\text{right}} R_{\text{bleeder}} + V_{\text{pwr}}}{R_1 + R_{\text{bleeder}}}$$

$$I_{\text{right}} = \frac{I_{\text{left}} R_{\text{bleeder}}}{R_{\text{bleeder}} + R_{\text{load}}}$$

Solve the above equations as a system, include other equations to get derived values

```

In [9]: 1 def evaluate(r1_ohms, rbleeder_ohms, rload_ohms):
2         return solve([
3             # solve for currents
4             left_mesh, right_mesh,
5
6             # bleeder is superposition of left and right mesh currents
7             # (which are in opposite directions)
8             Eq(ibleeder, ileft - iright),
9
10            # derive voltages
11            Eq(vab, vab_r1),
12            Eq(vbc, vbc_rbleeder),
13
14            # bleeder = 10% of load
15            Eq(ibleeder, 0.1 * iright),
16
17            # replace resistor symbols with resistance values
18            Eq(r1, r1_ohms),
19            Eq(rbleeder, rbleeder_ohms),
20            Eq(rload, rload_ohms),
21
22            # include power supply
23            Eq(vpwr, 15), # volts
24            ])[0]
25
26 values = evaluate(1.5e3, 30e3, 3e3)

```

Calculated Values

Load Current (A)	Bleeder Current (A)	A-B Voltage (V)	B-C Voltage (V)
3.23 m	322.58 μ	-5.32	-9.7

Measured Values

Load Current (A)	Bleeder Current (A)	A-B Voltage (V)	B-C Voltage (V)
2.98 m	300.00 μ	-6.03	-9.07

B: Current Divider Circuit

We designed a circuit which accepts a 15V power supply and delivers 10V to three parallel branches. It divides the current across those branches in a 1:2:3 ratio. It uses the following resistors:

In [10]:

```
1 r1 = 1e3
2 r2 = 10e3
3 r3 = 6.8e3
4 r4 = 3.9e3
5
6 r_bc = 1 / (1/r2 + 1/r3 + 1/r4)
7 r_total = r1 + r_bc
8 i_total = 15 / r_total
9 v_ab = 15 * r1 / r_total
10 v_bc = 15 * r_bc / r_total
11 print("V_ab =", f(v_ab, precision=2))
12 print("V_bc =", f(v_bc, precision=2))
13 print("I_tot =", f(i_total, precision=2))
```

V_ab = 5.02

V_bc = 9.98


I_tot = 5.02 m

In [11]:

```

1 cct = Circuit("""
2 V 1 11 {15}; down
3 W 1 1_1; up=0.5
4 W 3 3_1; up=0.5
5 P 1_1 3_1; right, v=5.02 V
6 R1 1 3 {1000}; right=3, a=R_1
7 W 3 4; down=1
8 W 4 5; left=1.5
9 W 4 6; right=1.5
10 R2 5 7 {10000}; down=1.5, a=R_2
11 R3 4 8 {6800}; down=1.5, a=R_3
12 R4 6 9 (3900); down=1.5, a=R_4
13 W 6 6_1; right=1.5
14 W 9 9_1; right=1.5
15 P 6_1 9_1; down, v=9.98 V
16 W 7 8; right
17 W 8 9; right
18 W 8 10; down=0.5
19 SW 11 10 no; right
20 A1 1; l=A, anchor=east
21 A2 3; l=B, anchor=west
22 A4 10; l=C, anchor=west
23 """)
24 cct.draw(label_ids=False, draw_nodes=False, label_nodes=False)

```

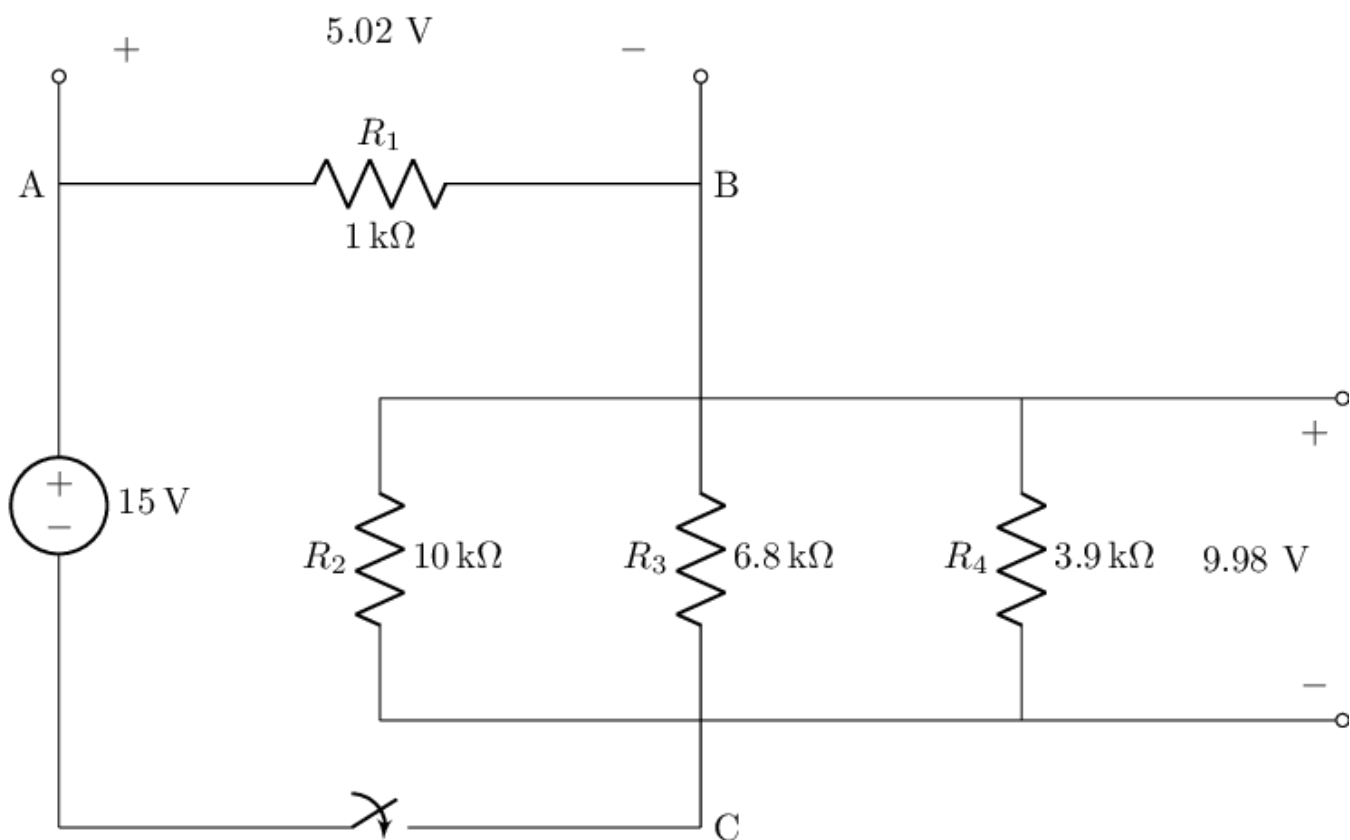

In [12]:

```

1 # proportion of current down branch
2 def current_parallel(resistor):
3     return i_total * r_bc / resistor

```

Calculated Values

Resistor	Current (A)	Current Ratio vs Current at R ₂
R ₂	997.7 μ	1.00

Resistor	Current (A)	Current Ratio vs Current at R ₂
R ₃	1.5 m	1.47
R ₄	2.6 m	2.56

Measured Values

Resistor	Current (A)	Current Ratio vs Current at R ₂
R ₂	1.11m	1.00
R ₃	1.42m	1.28
R ₄	2.52m	2.27